

University of California, Davis
Department of Electrical and Computer Engineering

EEEC180

DIGITAL SYSTEMS II

Winter Quarter 2024

LAB 2: Combinational Logic Design Using Verilog

Objective:

The purpose of this lab is to use Verilog to design combinational arithmetic circuits. You will also learn how to write self-checking testbenches.

Prelab - Behavioral vs. Structural RTL (15pts)

1. What is the difference between behavioral and structural HDL code?
2. Provide one small example (10 lines of code maximum) of a behavioral RTL module, and one small example of a structural RTL module.

Part 1 - Ripple-carry Adder (30 pts)

A *full adder* (FA) has inputs a , b and c_i (carry in) and produces outputs s (sum) and c_o (carry out).

$$c_o = a.b + a.c_i + b.c_i$$
$$s = a \oplus b \oplus c_i$$

An n -bit ripple-carry adder can be designed by connecting full-adders in a chain with the carry in for a given stage being the carry out of the previous stage and the carry in of the least significant bit being a 0.

 


Figure 1 - 8 bit Ripple Carry Adder

Perform the following steps:

1. Write a **behavioral** model for a full adder in Verilog. (Hint: an assign statement can describe each output equation.)
2. Instantiate your full adder subcircuit to build an *8-bit ripple-carry adder*. Add logic to produce an *Overflow* output, which should be set to 1 whenever the sum produced by the adder does not provide the correct signed (twos complement) value.

Perform the following steps:

1. Write a **structural** model in Verilog that describes an 4x4 unsigned array multiplier that can be implemented on the Altera DE10-Lite board. Use switches SW_{7-4} to represent the number A and switches SW_{3-0} to represent the number B. Display the hex value of A on HEX3 and the hex value of B on HEX2. Display the hex value of the result $P = A \times B$ on HEX1-0.
2. Modify the testbench for the adder to test the multiplier design. **Demonstrate your testbench to your TA.**
3. Compile your design in Quartus. Download your design to the Terasic DE10-Lite board and test your circuit. **Demonstrate your circuit to your TA.**

Part 3 - Generic Adder (25 pts)

Verilog *parameters* are a powerful way to create flexible HDL code. You should include parameters in your code wherever possible to allow reuse of modules by simply modifying parameters at instantiation. Helpful reference: <https://www.chipverify.com/verilog/verilog-parameters>.

Write a *generic* adder using Verilog parameters and generate statement in Verilog. Your adder should take a parameter K. See <https://www.chipverify.com/verilog/verilog-generate-block> for examples of how to use parameters and generate statements.

Update your testbench as well so that it works for any value of K. Demonstrate your testbench to your TA.

The TA will test your design for any value of K, such as K=7 or 11.

You don't have to download the design to the hardware for this part of the lab. You must show that the design works correctly via functional simulation and testbench.

Submission (100 pts total)

Submit the following items for verification and grading:

- Report containing
 - Page 1: Lab cover sheet with TA verifications for
 - 1) Prelab Q1 & Q2
 - 2) Part I – HW demonstration & testbench
 - 3) Part II – HW demonstration & testbench
 - 4) Part III – testbench
 - Prelab solution
 - Outputs and/or waveforms from self-checking testbenches for Pt I-III.
- Complete Verilog source code for all lab exercises including
 - partI.v, tb_partI.v
 - partII.v, tb_partII.v
 - partIII.v, tb_partIII.v
 - Any additional design files required to compile your ModelSim/Quartus projects.

Appendix - Self Checking Testbench

*A half adder has 2 inputs, so for exhaustive verification we must check the output for all the four input combinations, which can be done by the **for loop**.*

The testbench is self-checking – it examines the outputs and prints out an error message if the output is wrong.

```
module halfAdd (sum, cOut, a, b);
    output sum, cOut;
    input  a, b;

    xor      (sum, a, b);
    and      (cOut, a, b);
endmodule

module tBench;
    wire sum, co;
    reg [2:0] test;

    // design under test;
    halfAdd HA (sum, co, test[1], test[0]);
    // stimulus and verification that the output is correct
initial begin
    for (test = 0; test < 4; test = test + 1)
    begin
        #10;
        if ({co, sum} != (test[1] + test[0]))
            $display("ERROR: a=%b b=%b sum=%b cout=%b", test[1], test[0], sum, co);
        end
        #10 $finish;
    end
endmodule
```